



COMP 2280 - Introduction to Computer Systems

Module 5- Combinational Circuits

Introduction

- **Microprocessors contain millions of transistors**
 - AMD AM286 (1983): 134,000
 - AMD AM486 (1993): 1,185,000
 - Intel Pentium 4 (2000): 48 million
 - Intel core i7 quad (2008): 731 million
 - Intel i7 - 6 cores (2010): 2.27 billion
 - **AMD Ryzen 9 – 16 cores (2020): 19.2 billion**
- Logically, each transistor acts as a switch
 - Combined to implement logic functions AND, OR, NOT
 - Combined to build higher-level structures such as adders, multiplexers, decoders, registers, ...
 - Combined to build processor such as the LC-3

Introduction

- In digital design, we are concerned with designing and building circuits that work with binary data.
- We will start off by looking at very simple circuits and then building on top of them to get more complicated circuits.
- This will be a very brief introduction to design logic.
- Let's start off with the most basic of components that we need to build digital circuits: AND, OR, NOT, NOR, NAND.

Logic Gates

- **Perform logic functions:**
 - inversion (NOT), AND, OR, NAND, NOR, etc.
- **Single-input:**
 - NOT gate, buffer
- **Two-input:**
 - AND, OR, XOR, NAND, NOR, XNOR
- **Multiple-input**

Reference also found on Learn:


Boolean Algebra Basics

Two constants: 0 and 1

- 0 is equivalent to false
- 1 is equivalent to true

Operators		
Symbol	Description	Example
•	AND	$a \bullet b$
+	OR	$a + b$
–	NOT	\bar{a}
'	NOT	a'
\oplus	XOR (exclusive or)	$a \oplus b$

Single-Input Logic Gates

 

Note: The circle is important, we'll see it again with the negated/"NOT-versions" of the other gates


$$Y = \overline{A}$$

A	Y
0	1
1	0

Note: a line over an expression denotes negation

Two-Input Logic Gates


AND

 

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR

 


$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

More Two-Input Logic Gates


XOR

 

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


NAND

 

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOR

 

$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

XNOR

 


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Note the circles on the gates, and the lines over the expression

Multiple-Input Logic Gates


NOR3

 

$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

AND4

 

$$Y = ABCD$$


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

The Column for 'D' is missing but the output 'Y' is still only going to be true when all inputs are true

Multiple-Input Logic Gates

Note: Multi-input gates are equivalent to multiple two-input gates in series

 We draw a 3-input AND gate by combining two 2-input AND gates.



Classes of Digital Circuits

- Digital circuits can be classified as either
 - Combinational
 - Sequential
- Combinational circuits are those whose output depends only on the current inputs.
- Sequential circuits are those whose output depends on current inputs and its current state.

Combinational Circuits


- output depends on the current inputs only
- Stateless
- outputs are defined by Boolean functions of the inputs
- any combinational circuit can be implemented as a sum-of-products (SOP) or product-of-sums (POS)
- always gives 2 level circuits which are very fast.

Boolean Equations

- Functional specification of outputs in terms of inputs

- **Example:** $S = F(A, B, C_{in})$

$$C_{out} = F(A, B, C_{in})$$

 

$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

This may look complex, but you have already seen and used this Boolean equation.


Any ideas on what it is?

Boolean Equations

- Functional specification of outputs in terms of inputs

- **Example:** $S = F(A, B, C_{in})$

$$C_{out} = F(A, B, C_{in})$$

 

It's like a binary addition with the Carry-in and Carry-out bits!

$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

Truth Tables

- Truth tables specify the output of a circuit based on its inputs.
- Given a truth table, there are standard techniques for building a circuit that realizes the truth table.
- Two techniques
 - sum-of-products (SOP) technique
 - product-of-Sums (POS) Form
- Let's do a simple example.

Sum-of-Products (SOP) Form

- All equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a product (AND) of all input variables
- Each minterm is TRUE for that row (and only that row)
- Form function by ORing minterms where the output is TRUE
- Thus, a sum (OR) of products (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) = \overline{A}B + AB$$

- Aka: “List all possible ways for it to be True”

How to get a Minterm?

“With the current input on this row, how can I build an AND expression with NOTs that gives me TRUE?”

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a sum (OR) of all input variable
- Each maxterm is FALSE for that row (and only that row)
- Form function by ANDing the maxterms for which the output is FALSE
- Thus, a product (AND) of sums (OR terms)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

$$Y = F(A, B) = (A + B)(\overline{A} + B)$$

- Aka: “List (eliminate?) all possible ways for it to be False”

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You will only eat lunch (E):
 - If it's open (O) and
 - They **don't** serve corndogs (C)
 - Write a truth table for determining if you will eat lunch (E).

O	C	E
0	0	0
0	1	0
1	0	1
1	1	0

SOP & POS Form

- SOP – sum-of-products

O	C	E	minterm
0	0	0	$\overline{O} \overline{C}$
0	1	0	$\overline{O} C$
1	0	1	$O \overline{C}$
1	1	0	$O C$

$$Y = O\overline{C}$$

Aka: “List all possible ways for it to be True”

- POS – product-of-sums

O	C	E	maxterm
0	0	0	$O + C$
0	1	0	$O + \overline{C}$
1	0	1	$\overline{O} + C$
1	1	0	$\overline{O} + \overline{C}$

$$Y = (O + C)(O + \overline{C})(\overline{O} + \overline{C})$$

Aka: “List (eliminate?) all possible ways for it to be False”

Boolean Algebra

- Axioms and theorems to **simplify** Boolean equations
- Like regular algebra, but simpler: variables have only two values (1 or 0)
- **Duality** in axioms and theorems:
 - ANDs and ORs, 0's and 1's interchanged

Boolean Axioms

Axiom		Dual		Name
A1	$B = 0 \text{ if } B \neq 1$	A1'	$B = 1 \text{ if } B \neq 0$	Binary field
A2	$\overline{0} = 1$	A2'	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	A3'	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	A4'	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	A5'	$1 + 0 = 0 + 1 = 1$	AND/OR

Theorem		Dual		Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements



End of Part A

T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

B and 1 gives us B

B or 0 gives us B as well

 
 


T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

B and 0 gives us 0

B or 1 gives us 1

 
 


T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

B and B gives us B

B or B gives us B

  


T4: Involution Theorem

- $\overline{\overline{B}} = B$

The opposite of the opposite of
B is... B

$$\text{Not}(\text{Not}(B)) = B$$


 


T5: Complement Theorem

- $B \cdot \bar{B} = 0$
- $B + \bar{B} = 1$

B and NOT B is 0

B or NOT(B) is 1

  

Boolean Theorems Summary

	Theorem		Dual	Name
T1	$B \bullet 1 = B$	T1'	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	T2'	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	T3'	$B + B = B$	Idempotency
T4		$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	T5'	$B + \overline{B} = 1$	Complements

Boolean Theorems of Several Vars

Theorem		Dual		Name
T6	$B \bullet C = C \bullet B$	T6'	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	T7'	$(B + C) + D = B + (C + D)$	Associativity
T8	$(B \bullet C) + B \bullet D = B \bullet (C + D)$	T8'	$(B + C) \bullet (B + D) = B + (C \bullet D)$	Distributivity
T9	$B \bullet (B + C) = B$	T9'	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	T10'	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D)$ $= B \bullet C + \overline{B} \bullet D$	T11'	$(B + C) \bullet (\overline{B} + D) \bullet (C + D)$ $= (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B_0 \bullet B_1 \bullet B_2 \dots}$ $= (\overline{B_0} + \overline{B_1} + \overline{B_2} \dots)$	T12'	$\overline{B_0 + B_1 + B_2 \dots}$ $= (\overline{B_0} \bullet \overline{B_1} \bullet \overline{B_2})$	De Morgan's Theorem

Think Math Algebra

Simplifying Boolean Equations

Example 1:

- $Y = AB + \bar{A}B$

$$= B(A + \bar{A})$$

T8, Distributivity

We "factor out" the common term B

$$= B(1)$$

T5', Complements

A or Not(A), that is the question...

$$= B$$

T1, Identity

*B and 1, same as B*1*

Simplifying Boolean Equations

Example 2:

- $Y = A(AB + ABC)$

$$= A(AB(1 + C))$$

$$= A(AB(1))$$

$$= A(AB)$$

$$= (AA)B$$

$$= AB$$

T8, common term AB

T2', C or 1, always 1



T1, AB and 1, easy

T7, $A*(A*B)=(A*A)*B$

T3, A and A, redundant

DeMorgan's Theorem

 
 
- $Y = \overline{AB} = \overline{A} + \overline{B}$



I go camping when there are:
NOT (rain and thunderstorms)
NOT(rain) or NOT(thunderstorms)

A	B	Not(AB)	Not(A) + Not(B)
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

  - $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$





I go hiking when there are:
NOT(Wolves or Bears)
NOT(Wolves) and NOT(bears)

A	B	Not(A+B)	Not(A) * Not(B)
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

Bubble Pushing



- **Backward:**

- Body changes
- Adds bubbles to inputs

  


- **Forward:**

- Body changes
- Adds bubble to output

  


Bubble Pushing

 - What is the Boolean expression for this circuit?



Bubble Pushing

 
- What is the Boolean expression for this circuit?






$$Y = AB + CD$$

Bubble Pushing Rules

 - Begin at output, then work toward inputs
- Push bubbles on final output back
- Draw gates in a form so bubbles cancel




Bubble Pushing Example

   

$$Y = \overline{A}\overline{B}C + \overline{D}$$

From Logic to Gates

 
- Two-level logic: ANDs followed by ORs
- Example: $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$



Multiple-Output Circuits

 - **Example: Priority Circuit**


Output asserted
corresponding to
most significant
TRUE input



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0

Priority Circuit Hardware

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

 

Don't Cares

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0


A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

Some Common Circuits

- We now look at some common combinational circuits that are used in designing a CPU.
- These include: multiplexor, decoder and adders.

Multiplexer (Mux)

 
- Selects between one of N inputs to connect to output
- $\log_2 N$ -bit select input – control input
- Example: **2:1 Mux**



S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		


Multiplexer Implementations

- **Logic gates**

 


S	D_1	D_0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

S	Y
0	D_0
1	D_1

 


Decoders

 - N inputs, 2^N outputs
- One-hot outputs: only one output HIGH at once




A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Decoder Implementation

 


1-Bit Adders


Half Adder

 

A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


Full Adder

 

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

 

Alternate Drawings

Full Adder (1-bit addition)

 


C_{in}	A	B	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Multibit Adders (CPAs)

- Types of Carry Propagate Adders (CPAs):
 - Ripple-carry (slow but simple)
 - Carry-lookahead (fast)
 - Prefix (faster)
- Carry-lookahead and Prefix adders are faster for large adders with several bits, but require more hardware.

The Carry-lookahead and Prefix Adders are NOT in any labs, assignments, or tests


Symbol

 

The '/ N' denotes N input lines
In this case, N bits of A and B


Ripple-Carry Adder

 - Chain 1-bit adders together
- Carry “ripples” through entire chain
 - Ex: 0111 1111 1111 1111 + 1
- Disadvantage: **slow**




Ripple-Carry Adder - Example

 
- Let's add X to itself
- Let X be a 2-bit number, therefore: $X = X_1X_0$
- It just so happens that $X_1X_0 + X_1X_0 = X_1X_00$
- **Why? Could we take a shortcut?**



Ripple-Carry Adder - Shortcut

 


- **New and Improved:**

 


Subtractor

Symbol

 


Implementation

 

The '/ N' denotes N input lines
In this case, N bits of A and B


Logic Using Decoders

- Sum (OR) of Products (AND/minterms)

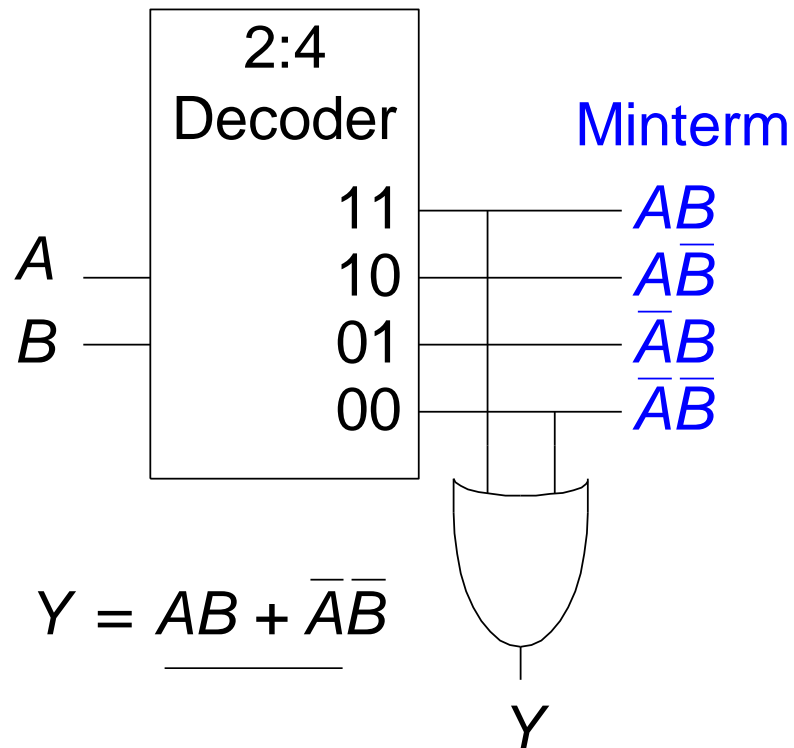

Programmable Logic Array (PLA)

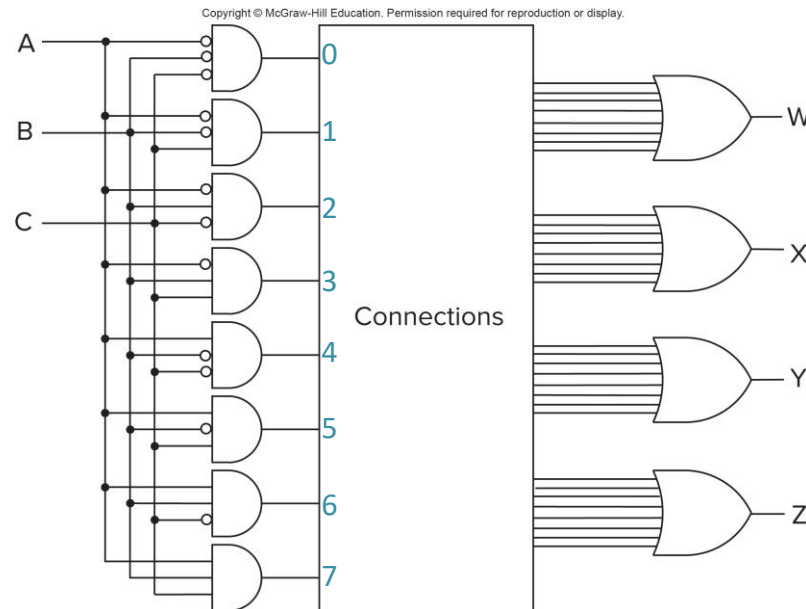- It is possible to build a logic circuit that uses logic circuits to decide what logic circuits to implement!



The Programmable Logic Array is NOT in any labs, assignments, or tests



*This PLA could, for instance, be used to build a 1-bit adder circuit by connecting **W** to outputs 3, 5, 6 & 7 = $C(i+1)$; and **X** to outputs 1, 2, 4, & 7 = $S(i)$.*

Timing Diagrams

- A **timing diagram** is a graphical representation of the input and output signals (values) of circuit, where the domain is time.
- Timing diagrams are used to illustrate how a circuit works and are useful for debugging circuits.
- Commercial debugging tools such as oscilloscopes and logic analyzers generate timing diagrams for circuits they are connected to.
- When drawing a timing diagram for a circuit, you should display all your inputs.
- You should display the outputs you want to examine in your diagram.

Timing Diagrams

We will discuss this diagram in class.

  

Timing Diagrams

- In reality, each gate introduces a slight delay in a circuit. You can draw these into your diagram if you want.
- These delays can sometimes cause glitches in circuits.
 - An output jumps momentarily from 0 to 1 and then back to 0,
or
 - An output jumps momentarily from 1 to 0 and then back to 1.
- These can be hard to debug, but can be dealt with by adding extra gates to the circuit.
- We will encounter timing diagrams throughout the course.